

Problem 1(40PTS):

Do the online tutorials:

<http://www.engr.sjsu.edu/~dparent/ICGROUP/UNIX.pdf>

and

http://www.engr.sjsu.edu/~dparent/ICGROUP/CDS_1.pdf

to either learn the basics of the tool or refresh your memory.

Problem 2(50PTS):

Design a CMOS inverter in **the tsmc .18 deep process** with the following specification:

tphl=tplh=30ps (with in 10%)

Cg=60fF

No layout required.

$$A := 10300\Omega \quad C_{JSWN} := 2.47 \cdot 10^{-12} \frac{F}{cm} \quad C_{JN} := 9.53 \cdot 10^{-8} \frac{F}{cm^2} \quad C_{GDON} := 8.35 \cdot 10^{-12} \frac{F}{cm}$$

$$L_N := .18 \cdot 10^{-4} cm \quad K_{EQ} := \frac{-2\sqrt{.84}}{-1.8} \cdot (\sqrt{.84 + 1.8} - \sqrt{.84}) \quad K_{EQ} = 0.721 \quad D_D := .36 \cdot 10^{-4} cm$$

$$C_g := 60 \cdot 10^{-15} F \quad N := 1 \quad N_{SN} := 1$$

$$\tau_{PHL} := .03 \cdot 10^{-9} s \quad M := 1 \quad N_{SP} := 1 \quad S := 1 \quad R := 2.16$$

$$W_N := \frac{C_g + C_{JSWN} \cdot 2 \cdot D_D \cdot K_{EQ} \cdot (N + M)}{\frac{\tau_{PHL}}{N_{SN} \cdot L_N \cdot A} - (N + M \cdot R) \cdot (C_{JSWN} \cdot 2 \cdot K_{EQ} + C_{JN} \cdot D_D \cdot K_{EQ} + 2 \cdot C_{GDON})}$$

$$W_N = 6.698 \times 10^{-4} cm$$

$$W_P := R \cdot W_N \quad W_P = 1.447 \times 10^{-3} cm$$

$$\tau_{\text{PHL}_M} := (39 - 5) \cdot 10^{-14} \text{ s}$$

$$\tau_{\text{PLH}_M} := (1037 - 1005) \cdot 10^{-12} \text{ s}$$

$$W_N := \frac{\tau_{\text{PHL}_M}}{\tau_{\text{PHL}}} \cdot W_N$$

$$W_N = 7.591 \times 10^{-4} \text{ cm}$$

$$\text{Error} := \frac{\tau_{\text{PHL}} - \tau_{\text{PHL}_M}}{\tau_{\text{PHL}}} \cdot 100$$

$$\text{Error} = -13.333$$

$$W_P := \frac{\tau_{\text{PLH}_M}}{\tau_{\text{PLH}}} \cdot W_P$$

$$W_P = 1.543 \times 10^{-3} \text{ cm}$$

$$\text{Error} := \frac{\tau_{\text{PLH}} - \tau_{\text{PLH}_M}}{\tau_{\text{PLH}}} \cdot 100$$

$$\text{Error} = -6.667$$

$$\tau_{\text{PHL}_M} := (36 - 5) \cdot 10^{-12} \text{ s}$$

$$\tau_{\text{PLH}_M} := (1036 - 1005) \cdot 10^{-12} \text{ s}$$

$$W_N := \frac{\tau_{\text{PHL}_M}}{\tau_{\text{PHL}}} \cdot W_N$$

$$W_N = 7.844 \times 10^{-4} \text{ cm}$$

$$\text{Error} := \frac{\tau_{\text{PHL}} - \tau_{\text{PHL}_M}}{\tau_{\text{PHL}}} \cdot 100$$

$$\text{Error} = -3.333$$

$$W_P := \frac{\tau_{\text{PLH}_M}}{\tau_{\text{PLH}}} \cdot W_P$$

$$W_P = 1.595 \times 10^{-3} \text{ cm}$$

$$\text{Error} := \frac{\tau_{\text{PLH}} - \tau_{\text{PLH}_M}}{\tau_{\text{PLH}}} \cdot 100$$

$$\text{Error} = -3.333$$

Problem 3(10PTS):

Develop a Model for a 2 input NAND gate (worst or slowest case) for **the tsmc .18 deep process.**

Find A and R.

A=7070 ohms and R=1.45, for a trise=tfall of input=10ps

		TPM	TPS	ERROR	W old	W new
53	5	48	70	-31.4286	3.68	2.523429
1069	1005	64	70	-8.57143	3.98	3.638857
65.68	5	60.68	70	-13.3143	2.523429	2.187452
1065.5	1005	60.5	70	-13.5714	3.638857	3.145012
69	5	64	70	-8.57143	2.187452	1.999956
1069.5	1005	64.5	70	-7.85714	3.145012	2.897904
71.74	5	66.74	70	-4.65714	1.999956	1.906815
1071.7	1005	66.7	70	-4.71429	2.897904	2.761289
73.15	5	68.15	70	-2.64286	1.906815	1.856421
1073.4	1005	68.4	70	-2.28571	2.761289	2.698173
74.11	5	69.11	70	-1.27143	1.856421	1.832818
1074	1005	69	70	-1.42857	2.698173	2.659628
74.49	5	69.49	70	-0.72857	1.832818	1.819465
1074.6	1005	69.6	70	-0.57143	2.659628	2.64443

$$A := 7070\Omega \quad C_{JSWN} := 2.47 \cdot 10^{-12} \frac{F}{cm} \quad C_{JN} := 9.53 \cdot 10^{-8} \frac{F}{cm^2} \quad C_{GDON} := 8.35 \cdot 10^{-12} \frac{F}{cm}$$

$$L_N := .18 \cdot 10^{-4} cm \quad K_{EQ} := \frac{-2\sqrt{.84}}{-1.8} \cdot (\sqrt{.84 + 1.8} - \sqrt{.84}) \quad K_{EQ} = 0.721 \quad D_D := .36 \cdot 10^{-4} cm$$

$$C_g := 25 \cdot 10^{-15} F \quad N := 3 \quad N_{SN} := 2$$

$$\tau_{PHL} := .07 \cdot 10^{-9} s \quad M := 2 \quad N_{SP} := 1 \quad S := 1 \quad R := 1.45$$

$$W_N := \frac{C_g + C_{JSWN} \cdot 2 \cdot D_D \cdot K_{EQ} \cdot (N + M)}{\frac{\tau_{PHL}}{N_{SN} \cdot L_N \cdot A} - (N + M \cdot R) \cdot (C_{JSWN} \cdot 2 \cdot K_{EQ} + C_{JN} \cdot D_D \cdot K_{EQ} + 2 \cdot C_{GDON})}$$

$$W_N = 1.82 \times 10^{-4} cm$$

$$W_P := R \cdot W_N \quad W_P = 2.639 \times 10^{-4} cm$$

Verify the model for various loads and a 3 input NAND gate.

$$A := 7070\Omega \quad C_{JSWN} := 2.47 \cdot 10^{-12} \frac{F}{cm} \quad C_{JN} := 9.53 \cdot 10^{-8} \frac{F}{cm^2} \quad C_{GDON} := 8.35 \cdot 10^{-12} \frac{F}{cm}$$

$$L_N := .18 \cdot 10^{-4} cm \quad K_{EQ} := \frac{-2\sqrt{.84}}{-1.8} \cdot (\sqrt{.84 + 1.8} - \sqrt{.84}) \quad K_{EQ} = 0.721 \quad D_D := .36 \cdot 10^{-4} cm$$

$$C_g := 25 \cdot 10^{-15} F \quad N := 3 \quad N_{SN} := 2$$

$$\tau_{PHL} := .1 \cdot 10^{-9} s \quad M := 2 \quad N_{SP} := 1 \quad S := 1 \quad R := 1.45$$

$$W_N := \frac{C_g + C_{JSWN} \cdot 2 \cdot D_D \cdot K_{EQ} \cdot (N + M)}{\frac{\tau_{PHL}}{N_{SN} \cdot L_N \cdot A} - (N + M \cdot R) \cdot (C_{JSWN} \cdot 2 \cdot K_{EQ} + C_{JN} \cdot D_D \cdot K_{EQ} + 2 \cdot C_{GDON})}$$

$$W_N = 9.91 \times 10^{-5} cm$$

$$W_P := R \cdot W_N \quad W_P = 1.437 \times 10^{-4} cm \quad \tau_{PLH} := \tau_{PHL}$$

$$\tau_{PHL_M} := (100 - 5) \cdot 10^{-12} s \quad \text{Error} := \frac{\tau_{PHL} - \tau_{PHL_M}}{\tau_{PHL}} \cdot 100 \quad \text{Error} = 5$$

$$\tau_{PLH_M} := (1010 - 1005) \cdot 10^{-12} s \quad \text{Error} := \frac{\tau_{PLH} - \tau_{PLH_M}}{\tau_{PLH}} \cdot 100 \quad \text{Error} = 5$$

$$A := 7070\Omega \quad C_{JSWN} := 2.47 \cdot 10^{-12} \frac{F}{cm} \quad C_{JN} := 9.53 \cdot 10^{-8} \frac{F}{cm^2} \quad C_{GDON} := 8.35 \cdot 10^{-12} \frac{F}{cm}$$

$$L_N := .18 \cdot 10^{-4} cm \quad K_{EQ} := \frac{-2\sqrt{.84}}{-1.8} \cdot (\sqrt{.84 + 1.8} - \sqrt{.84}) \quad K_{EQ} = 0.721 \quad D_D := .36 \cdot 10^{-4} cm$$

$$C_g := 50 \cdot 10^{-15} F \quad N := 3 \quad N_{SN} := 2$$

$$\tau_{PHL} := .055 \cdot 10^{-9} s \quad M := 2 \quad N_{SP} := 1 \quad S := 1 \quad R := 1.45$$

$$W_N := \frac{C_g + C_{JSWN} \cdot 2 \cdot D_D \cdot K_{EQ} \cdot (N + M)}{\frac{\tau_{PHL}}{N_{SN} \cdot L_N \cdot A} - (N + M \cdot R) \cdot (C_{JSWN} \cdot 2 \cdot K_{EQ} + C_{JN} \cdot D_D \cdot K_{EQ} + 2 \cdot C_{GDON})}$$

$$W_N = 6.18 \times 10^{-4} cm$$

$$W_P := R \cdot W_N \quad W_P = 8.961 \times 10^{-4} cm$$

$$\tau_{PLH} := \tau_{PHL}$$

$$\tau_{PHL_M} := (61 - 5) \cdot 10^{-12} s$$

$$\text{Error} := \frac{\tau_{PHL} - \tau_{PHL_M}}{\tau_{PHL}} \cdot 100 \quad \text{Error} = -1.818$$

$$\tau_{PLH_M} := (1060 - 1005) \cdot 10^{-12} s$$

$$\text{Error} := \frac{\tau_{PLH} - \tau_{PLH_M}}{\tau_{PLH}} \cdot 100 \quad \text{Error} = 1.175 \times 10^{-14}$$

$$A := 7070\Omega \quad C_{JSWN} := 2.47 \cdot 10^{-12} \frac{F}{cm} \quad C_{JN} := 9.53 \cdot 10^{-8} \frac{F}{cm^2} \quad C_{GDON} := 8.35 \cdot 10^{-12} \frac{F}{cm}$$

$$L_N := .18 \cdot 10^{-4} cm \quad K_{EQ} := \frac{-2\sqrt{.84}}{-1.8} \cdot (\sqrt{.84 + 1.8} - \sqrt{.84}) \quad K_{EQ} = 0.721 \quad D_D := .36 \cdot 10^{-4} cm$$

$$C_g := 25 \cdot 10^{-15} F \quad N := 5 \quad N_{SN} := 3$$

$$\tau_{PHL} := .15 \cdot 10^{-9} s \quad M := 3 \quad N_{SP} := 1 \quad S := 1 \quad R := 1.45$$

+

$$W_N := \frac{C_g + C_{JSWN} \cdot 2 \cdot D_D \cdot K_{EQ} \cdot (N + M)}{\frac{\tau_{PHL}}{N_{SN} \cdot L_N \cdot A} - (N + M \cdot R) \cdot (C_{JSWN} \cdot 2 \cdot K_{EQ} + C_{JN} \cdot D_D \cdot K_{EQ} + 2 \cdot C_{GDON})}$$

$$W_N = 1.444 \times 10^{-4} cm$$

$$W_P := R \cdot W_N \quad W_P = 2.093 \times 10^{-4} cm$$

$$\tau_{PLH} := \tau_{PHL}$$

$$\tau_{PHL_M} := (83 - 5) \cdot 10^{-12} s$$

$$Error := \frac{\tau_{PHL} - \tau_{PHL_M}}{\tau_{PHL}} \cdot 100 \quad Error = 48$$

$$\tau_{PLH_M} := (1083 - 1005) \cdot 10^{-12} s$$

$$Error := \frac{\tau_{PLH} - \tau_{PLH_M}}{\tau_{PLH}} \cdot 100 \quad Error = 48$$

		TPM	TPS	ERROR	W old	W new	
62	5	57	100	-43	5.276	3.00732	
1101	1005	96	100	-4	7.65	7.344	
120	5	115	100	15	3.00732	3.458418	
1054	1005	49	100	-51	7.344	3.59856	
84	5	79	100	-21	3.458418	2.73215	
1089	1005	84	100	-16	3.59856	3.02279	
92	5	87	100	-13	2.73215	2.376971	
1092	1005	87	100	-13	3.02279	2.629828	
96	5	91	100	-9	2.376971	2.163043	
1097	1005	92	100	-8	2.629828	2.419441	
100	+	5	95	100	-5	2.163043	2.054891
1100	1005	95	100	-5	2.419441	2.298469	
102	5	97	100	-3	2.054891	1.993244	
1102	1005	97	100	-3	2.298469	2.229515	
104	5	99	100	-1	1.993244	1.973312	
1103	1005	98	100	-2	2.229515	2.184925	

$$A := 5750\Omega \quad C_{J\text{SWN}} := 2.47 \cdot 10^{-12} \frac{\text{F}}{\text{cm}} \quad C_{J\text{N}} := 9.53 \cdot 10^{-8} \frac{\text{F}}{\text{cm}^2} \quad C_{\text{GDON}} := 8.35 \cdot 10^{-12} \frac{\text{F}}{\text{cm}}$$

$$L_{\text{N}} := .18 \cdot 10^{-4} \text{cm} \quad K_{\text{EQ}} := \frac{-2\sqrt{.84}}{-1.8} \cdot (\sqrt{.84 + 1.8} - \sqrt{.84}) \quad K_{\text{EQ}} = 0.721 \quad D_{\text{D}} := .36 \cdot 10^{-4} \text{cm}$$

$$C_{\text{g}} := 25 \cdot 10^{-15} \text{F} \quad N := 5 \quad N_{\text{SN}} := 3$$

$$\tau_{\text{PHL}} := .1 \cdot 10^{-9} \text{s} \quad M := 3 \quad N_{\text{SP}} := 1 \quad S := 1 \quad R := 1.12$$

$$W_{\text{N}} := \frac{C_{\text{g}} + C_{\text{JSWN}} \cdot 2 \cdot D_{\text{D}} \cdot K_{\text{EQ}} \cdot (N + M)}{\frac{\tau_{\text{PHL}}}{N_{\text{SN}} \cdot L_{\text{N}} \cdot A} - (N + M \cdot R) \cdot (C_{\text{JSWN}} \cdot 2 \cdot K_{\text{EQ}} + C_{\text{JN}} \cdot D_{\text{D}} \cdot K_{\text{EQ}} + 2 \cdot C_{\text{GDON}})}$$

$$W_{\text{N}} = 1.972 \times 10^{-4} \text{cm}$$

$$W_{\text{P}} := R \cdot W_{\text{N}} \quad W_{\text{P}} = 2.209 \times 10^{-4} \text{cm} \quad \tau_{\text{PLH}} := \tau_{\text{PHL}}$$

A and R are different for the inverter, nand2, and nand3 because the effective channel length is increasing with these gates, and thus the electric field is reduced, which reduced the electric field so we switch from $(v_{\text{g}} - v_{\text{t}})$ to $(v_{\text{g}} - v_{\text{t}})^2$ relationship.

Explain why A and R are different for the inverter and the nand.

Problem 3(10PTS):

Label each section of the ID graph as being in sub threshold, saturation, and velocity saturation.

Write down the generic equations for each area of operation.

Describe why each area of the graph follows the generic equation.

Redraw the graph if L was increased by 3 times

sub threshold follows a “BJT” like dependence based on diffusion.
 Normal saturation follows $(V_g - V_t)^2$, and velocity saturation follows $(V_g - V_t)$
 because the un x E field linear relationship no longer holds because the carries
 are bouncing off the lattice.

